

**EEL3060**

**Power Engineering Lab**



---

**Determination of the Sequence Reactances of an Alternator**

---

**Professor:** Dr. Ravi Yadav

**By:**

<b>Name</b>	<b>Roll Number</b>
Dhyey Findoriya	B22EE024

## I. Objective

To determine sequence reactances of a three-phase alternator.

## II. Apparatus

- 3-phase Alternator (3kVA)
- Ammeter
- Armature Rheostat (15A, 50  $\Omega$ )
- Field Rheostat (2.8A, 290  $\Omega$ )
- DC Motor
  - 1500 rpm
  - Armature Voltage - 220 V
  - Armature Current - 20 A
  - Field Voltage - 220 V
  - Field Current - 1.65 A
- Multimeter
- Connecting Wires
- 3-phase Power Supply (Auto Transformer/Variac)

## III. Theory

### 1. Positive Sequence Impedance ( $Z_1$ )

- The positive sequence reactance of a three-phase alternator is equal to the synchronous reactance ( $X_s$ ) determined by open-circuit and short-circuit tests.
- Formula:  $X_1 = X_s$ .

### 2. Negative Sequence Impedance ( $Z_2$ )

- It is found by applying a balanced negative sequence voltage to the armature terminals while the machine runs at synchronous speed with the field winding short-circuited.
- The ratio of phase voltage ( $V_{ph}$ ) to phase current ( $I_{ph}$ ) gives the negative sequence impedance ( $Z_2$ ):

$$Z_2 = \frac{V}{I}$$

$$X_2 = \sqrt{Z_2^2 - R_a^2}$$

where  $R_a$  (Armature resistance) is given by:

$$R_a = 1.2 \times R_m$$

( $R_m$  = measured phase resistance)

### 3. Zero Sequence Impedance ( $Z_0$ )

- Determined by connecting the three-phase armature windings in parallel to a single-phase source while keeping the machine at synchronous speed with field winding shorted.
- The zero sequence impedance ( $Z_0$ ) is given by:

$$Z_0 = \frac{3V}{I}$$

$$X_0 = \sqrt{Z_0^2 - R_a^2}$$

## IV. Experimental Procedure

### a) Negative Sequence Impedance Measurement

Steps:

#### 1. Circuit Setup:

- Connect the circuit as shown in Figure 1. (Circuit Diagram for Negative Sequence Impedance Measurement.)

#### 2. Applying Voltage:

- Run the DC motor to maintain synchronous speed.
- Apply voltage to the stator windings while keeping the speed constant.

#### 3. Measurement:

- $R_m = 1.6\Omega$
- Record the readings of the voltmeter and ammeter.
- Take 3-4 readings for different applied voltages.
- Ensure that the armature current does not exceed its rated value at any voltage.

#### 4. Calculations:

- For each reading, calculate the negative sequence impedance using the following formula:

$$Z_2 = \frac{V}{I}$$

$$X_2 = \sqrt{Z_2^2 - R_a^2}$$

- Finally, calculate the average of the three  $Z_2$  values to determine the final negative sequence impedance.

### Circuit Diagram

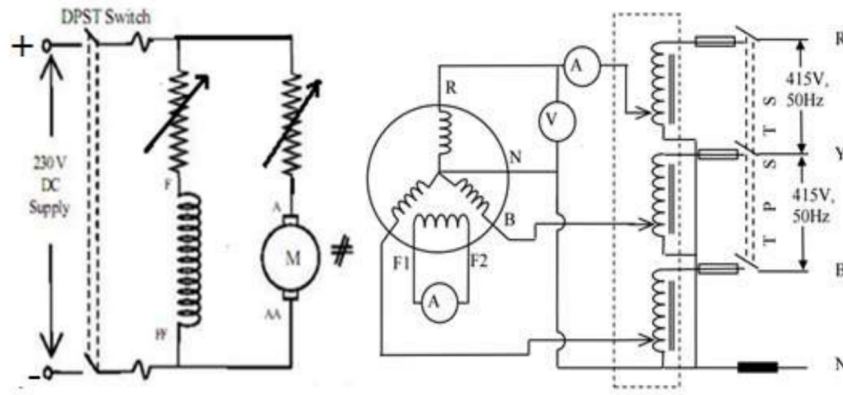


Figure 1: Circuit Diagram for Negative Sequence Impedance( $Z_2$ ) Measurement

### Observation Table

S. No.	$V(V)$	$I(A)$	$Z_2(\Omega)$
1	5.23	1.00	5.23
2	10.41	1.80	5.78
3	15.92	3.00	5.31
4	23.19	4.26	5.32

Table 1: Observation Table for Negative Sequence Impedance

### Calculations

1. For the first measurement:

$$Z_2 = \frac{V}{I} = \frac{5.23}{1.00} = 5.23 \Omega$$

2. For the second measurement:

$$Z_2 = \frac{V}{I} = \frac{10.41}{1.80} = 5.78 \Omega$$

3. For the third measurement:

$$Z_2 = \frac{V}{I} = \frac{15.92}{3.00} = 5.31 \Omega$$

4. For the fourth measurement:

$$Z_2 = \frac{V}{I} = \frac{23.19}{4.26} = 5.32 \Omega$$

Now, to calculate the average  $Z_2$ :

$$\text{Average } Z_2 = \frac{Z_2(1) + Z_2(2) + Z_2(3) + Z_2(4)}{4} = \frac{5.23 + 5.78 + 5.31 + 5.32}{4} = 5.41 \Omega$$

$$R_m = 1.2 * R_m = 1.2 * 1.6 = 1.92 \Omega$$

$$X_2 = \sqrt{Z_2^2 - R_a^2} = \sqrt{5.41^2 - 1.92^2} = 5.058 \Omega$$

## b) Zero Sequence Impedance Measurement

### Steps:

#### 1. Circuit Setup:

- Connect the circuit as shown in Figure 2. (Circuit Diagram for Zero Sequence Impedance Measurement.)

#### 2. Applying Voltage:

- Keep the synchronous machine at a standstill.
- Switch on the power supply.

#### 3. Measurement:

- $R_m = 1.6 \Omega$
- Gradually increase the input voltage and record the voltmeter and ammeter readings.
- Repeat for different voltages (below rated voltage and below rated current).

#### 4. Calculations:

- For each reading, calculate the negative sequence impedance using the following formula:

$$Z_0 = \frac{3V}{I}$$

$$X_0 = \sqrt{Z_0^2 - R_a^2}$$

- Finally, calculate the average of the three  $Z_0$  values to determine the final negative sequence impedance.

### Circuit Diagram

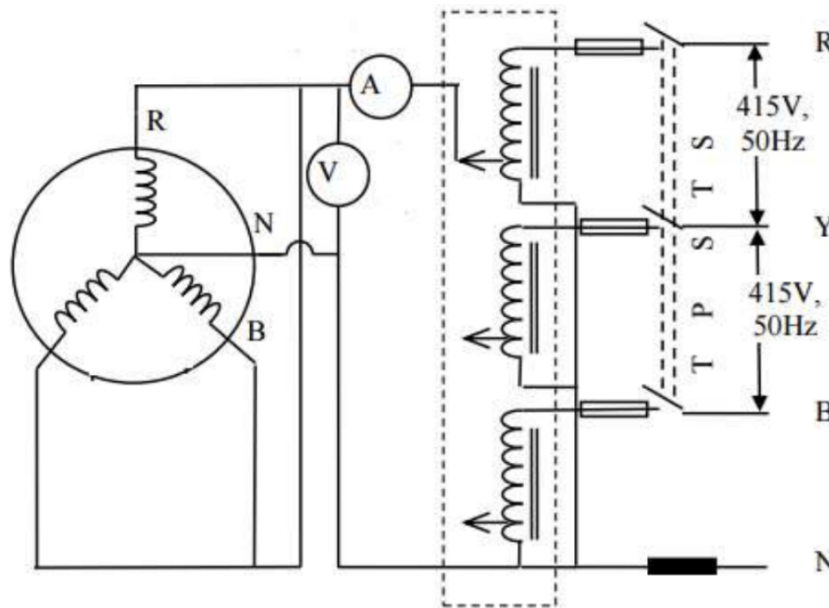


Figure 2: Circuit Diagram for Zero Sequence Impedance( $Z_0$ ) Measurement

### Observation Table

S. No.	V(V)	I(A)	$Z_0(\Omega)$
1	3.46	2.56	4.05
2	4.36	3.24	4.04
3	5.80	4.24	4.10

Table 2: Observation Table for Zero Sequence Impedance

## Calculations

1. For the first measurement:

$$Z_0 = \frac{3V}{I} = \frac{3 * 3.46}{2.56} = 4.05 \Omega$$

2. For the second measurement:

$$Z_0 = \frac{3V}{I} = \frac{3 * 4.36}{3.24} = 4.04 \Omega$$

3. For the third measurement:

$$Z_0 = \frac{3V}{I} = \frac{3 * 5.80}{4.24} = 4.10 \Omega$$

Now, to calculate the average  $Z_0$ :

$$\text{Average } Z_0 = \frac{Z_0(1) + Z_0(2) + Z_0(3)}{3} = \frac{4.04 + 4.05 + 4.10}{3} = 4.06 \Omega$$

$$R_a = 1.2 * R_m = 1.2 * 1.6 = 1.92 \Omega$$

$$X_0 = \sqrt{Z_0^2 - R_a^2} = \sqrt{4.06^2 - 1.92^2} = 3.577 \Omega$$

## V. Results & Conclusion

- The positive sequence reactance of a three-phase alternator is equal to the synchronous reactance ( $X_s$ ) determined by open-circuit and short-circuit tests.
- The negative sequence reactance ( $X_2$ ) was calculated by applying a balanced negative sequence voltage to the alternator, and its impedance was found using the measured voltage and current.
- The zero sequence reactance ( $X_0$ ) was determined by connecting all armature windings in parallel and measuring the response to a single-phase supply.
- These values are crucial for understanding how an alternator behaves under unbalanced and fault conditions, which helps in designing protective measures and ensuring system stability.
- The experiment successfully demonstrated the measurement techniques for sequence reactances, reinforcing their importance in power system analysis and fault diagnosis.